

MERIT PAPER – 01 SCHEME

01) 1

02) 5

03) 4

04) 5

05) 1

06) 3

07) 1- Customer

2- Customer Details

3- Supplier

4- Payment or Invoice

5- Preparing and Agreeing estimate

6- Agreed estimate


7- Materials provided

8- Job Schedule

9- Start date confirmation

10- Customer Name

08)

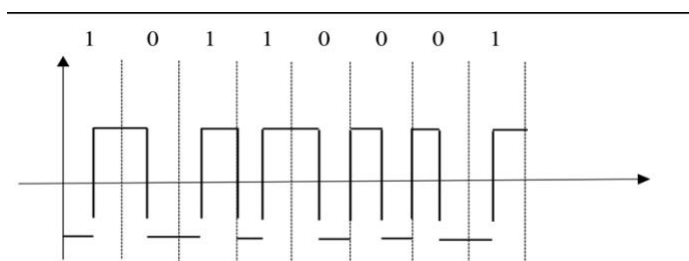


09) (i) The combinational circuit has one output, it generates and doesn't depend on any of its previous inputs

Sequential circuits are the ones that depend on past as well as previous inputs for generating output.

(ii) $Q - 1$

$Q' - 0$

10) a) i)

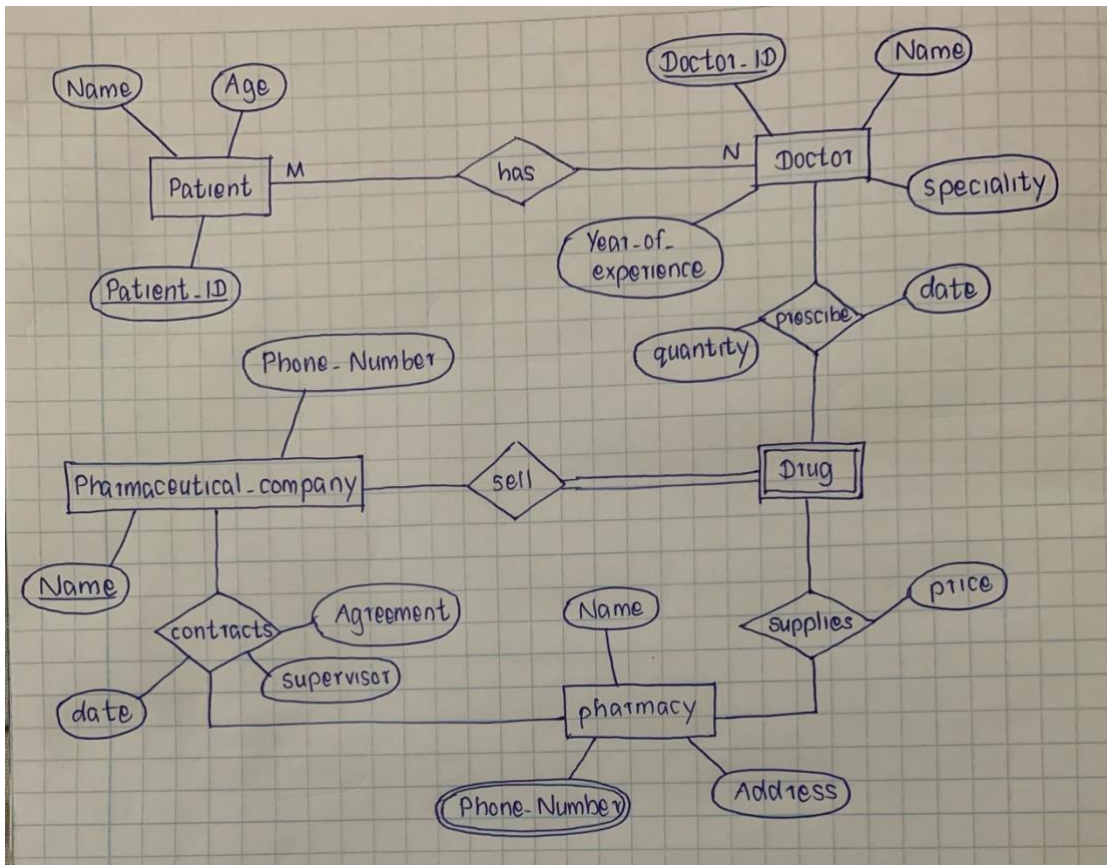

ii)

